

CSA1280 – COMPUTER ARCHITECTURE

EXPERIMENT – 32

FULL ADDER USING NAND GATES

AIM: To design and implement a Full Adder using NAND gates circuit using Logisim simulator.

ALGORITHM

1. Open the **Logisim** simulator.
2. Place three input pins: A, B, and Cin.
3. Use NAND gates to construct the **Sum** and **Carry** outputs.
4. Implement the Sum as $A \oplus B \oplus \text{Cin}$.
5. Implement the Carry as $AB + \text{BCin} + \text{ACin}$.
6. Connect the outputs to Sum (S) and Carry-out (Cout).
7. Test all possible input combinations.
8. Verify the outputs using the truth table.

Truth Table:

A	B	Cin	Sum (S)	Carry-out (Cout)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum:

$$S = A \oplus B \oplus \text{Cin}$$

Carry:

$$\text{Cout} = AB + BC_{in} + AC_{in}$$

RESULT:

